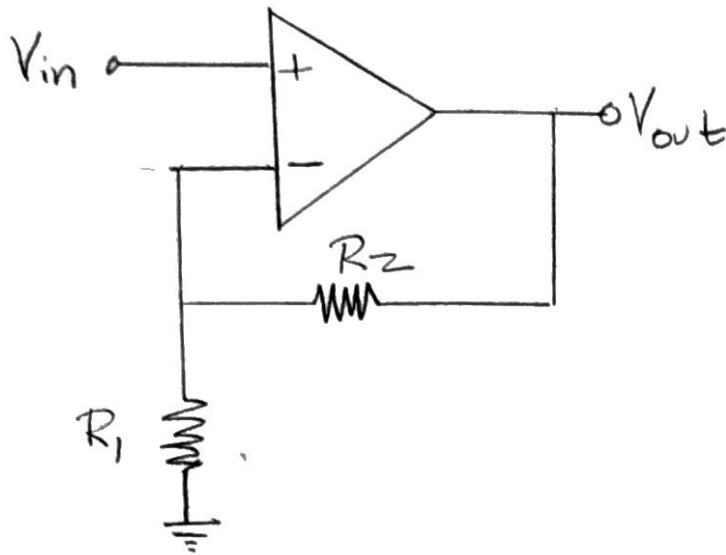


Op-Amp in Non-Inverting Configuration



The voltage on the $-$ input is

$$V_- = V_{out} \frac{R_1}{R_1 + R_2}$$

We also know $(V_{in} - V_-) B = V_{out}$ ↙ a big number

We want to know V_{out} in terms of V_{in} .


$$\left(V_{in} - V_{out} \frac{R_1}{R_1 + R_2} \right) B = V_{out}$$

Gain just V_{in} .
as claimed
by Mims
on p. 72

or $V_{out} \left(1 + B \frac{R_1}{R_1 + R_2} \right) = B V_{in}$

or $V_{out} = \frac{B V_{in}}{1 + B \frac{R_1}{R_1 + R_2}} \approx \frac{R_1 + R_2}{R_1} V_{in} = \left(1 + \frac{R_2}{R_1} \right) V_{in}$

Op-Amp in Inverting Configuration

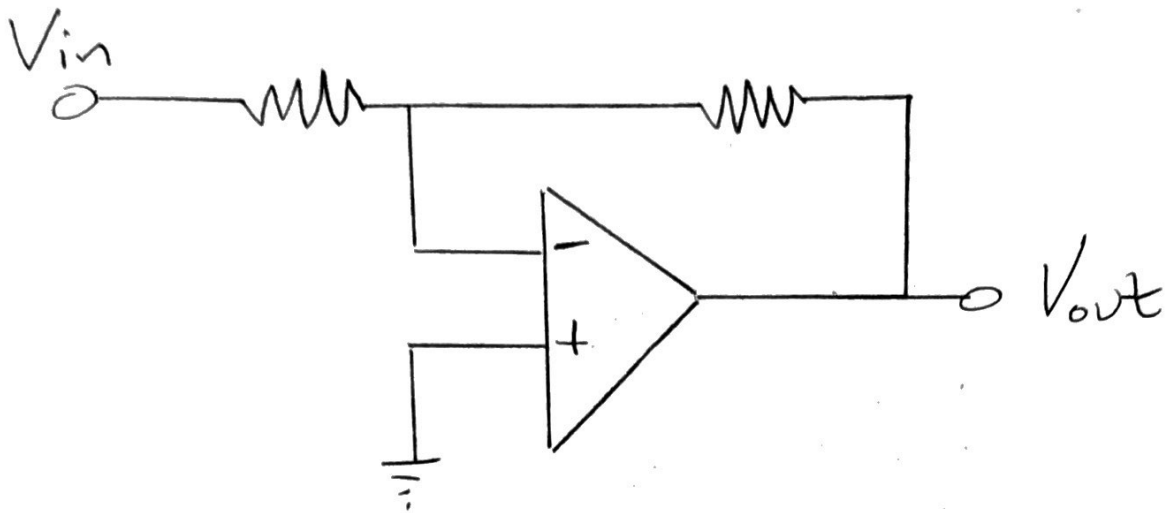

$$V_- = V_{in} + \frac{R_1}{R_1 + R_2} (V_{out} - V_{in}) = \frac{R_2}{R_1 + R_2} V_{in}$$

also

$$V_{out} = (V_+ - V_-) B$$

negligible compared to anything multiplied by B!

$$\Rightarrow V_- = 0$$

$$\Rightarrow R_2 V_{in} + R_1 V_{out} = 0$$

$$\Rightarrow V_{out} = -\frac{R_2}{R_1} V_{in}$$